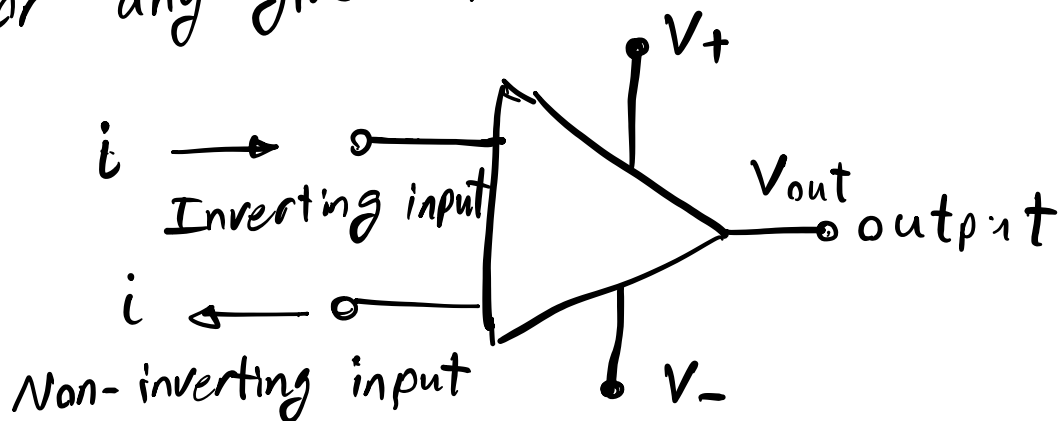


# Operational Amplifiers

## Introduction

An operational Amplifier, usually referred to as op-Amp, is a DC-coupled high-gain electronic voltage amplifier with two differential inputs and a single output. In its normal operation, the output of the op-Amp is controlled by negative feedback which, due to the amplifier's high gain, will completely control the output voltage for any given input.



## Ideal op-Amp

The ideal op-Amp has the following characteristics:

- Infinite voltage gain
- Infinite input impedance
- Zero output impedance
- Infinite bandwidth
- Zero input offset voltage


In a typical op-Amp, the circuit has characteristics close to the ideal one.

## A comparison between an ideal and a typical op Amp

Parameter	Ideal	Typical
Differential voltage gain	$\infty$	$10^5 - 10^9$
Voltage gain	0	$10^{-5}$
Gain bandwidth	$\infty$	1-20 MHz
Input impedance	$\infty$	$10^6 \Omega - 10^{12} \Omega$
output impedance	0	100 - 1000 $\Omega$

The output voltage is a function of the differential input voltage times the gain of the amplifier.

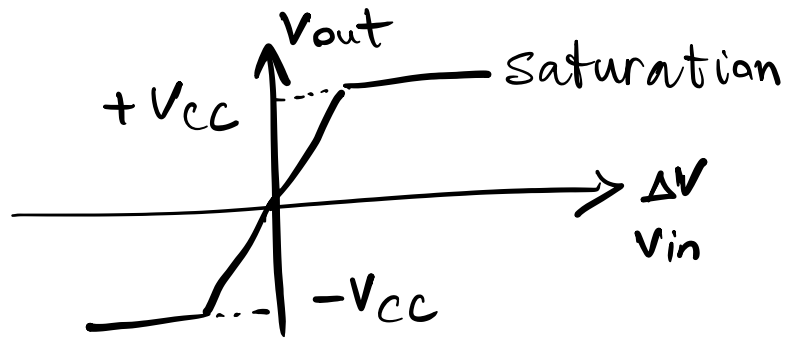The output voltage saturates to the supply source voltage:



---

## op-Amp rules :

- The voltage rule:

The output attempts to do whatever is necessary to make the voltage difference between the inputs zero.

- The current rule:

The inputs draw no current.

Comments on rule 1: The voltage gain of a real op-Amp is so high

that a fraction of a mV input will swing the output over its full range.


Comment on rule 2: The input current is so low ( $0.08 \mu\text{A}$ ).

---
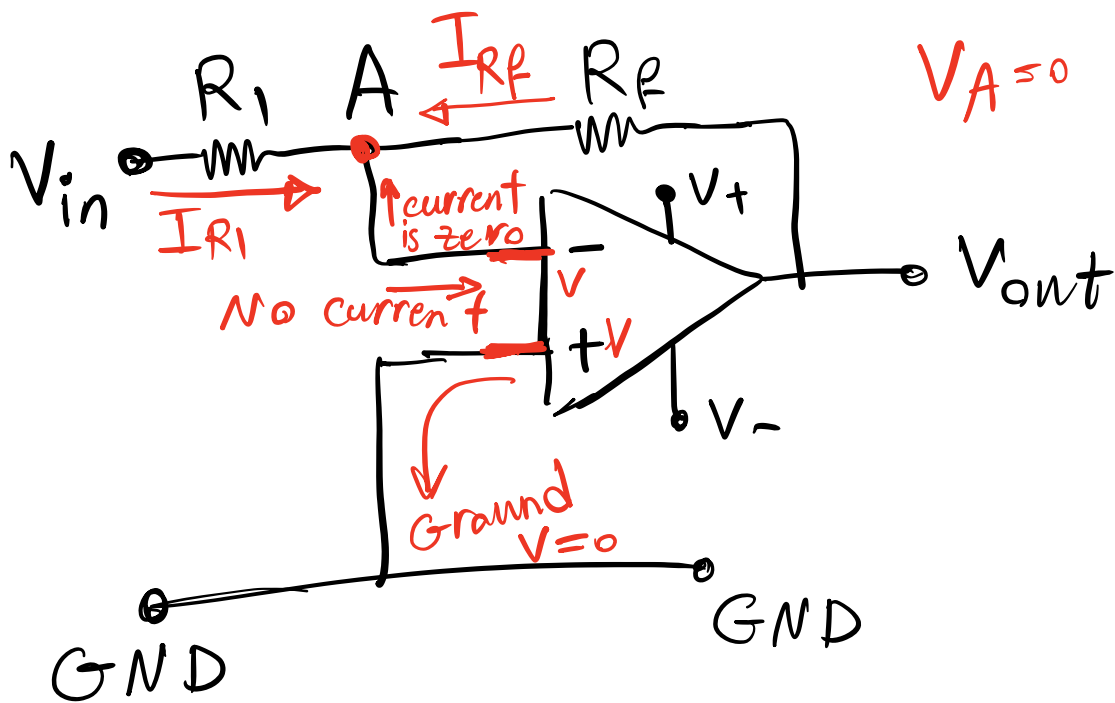
## Inverting Amplifier

The behaviour of most configurations of Op-Amps can be determined by applying the "Op-Amp" rules.

For an inverting amplifier, the current rule tries to drive the current to zero at point A.



$$I_{R_1} = \frac{V_{in}}{R_1} \quad I_{R_F} = \frac{V_{out}}{R_F}$$

$$I_{R_f} + I_{R_1} = 0$$

$$I_{R_f} = -I_{R_1}$$


$$\frac{V_{out}}{R_f} = -\frac{V_{in}}{R_1}$$

$$\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_1}$$
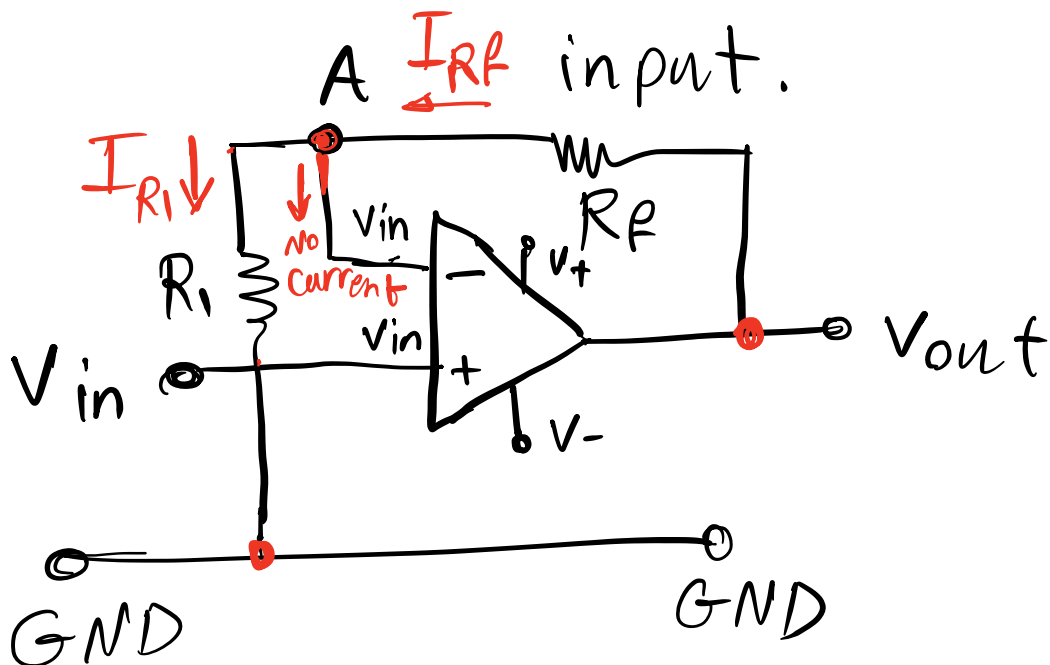
# Non-Inverting amplifier.

Current rule  $\rightarrow$  drive the current to zero at point A

Voltage rule  $\rightarrow$  Make the voltage At A equal to the input.





$$I_{R_1} = \frac{V_{in}}{R_1}$$


$$I_{R_f} = \frac{V_{out} - V_{in}}{R_f}$$

$$I_{R_1} = I_{R_f}$$

$$\frac{V_{in}}{R_1} = \frac{V_{out} - V_{in}}{R_f}$$

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_1}$$

# Summing amplifier

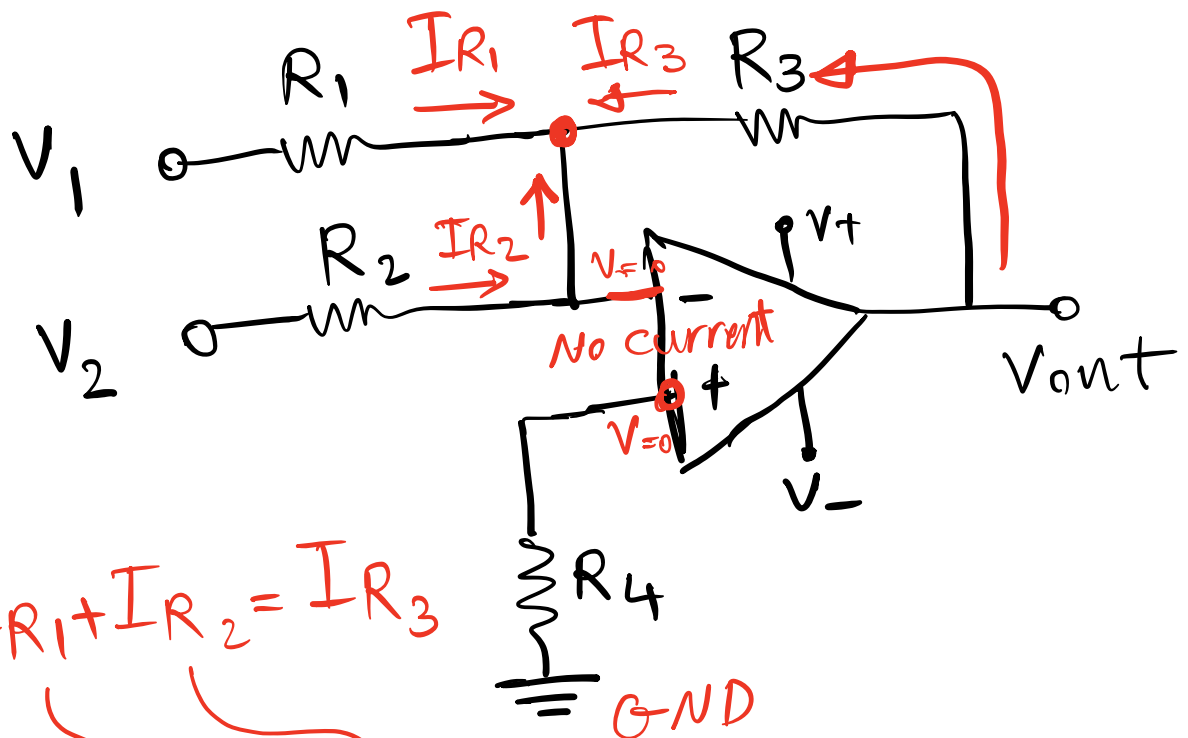


$$I_{R_1} + I_{R_2} = I_{R_3}$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = - \frac{V_{out}}{R_3}$$

$$R_1 = R_2 = R_3 \Rightarrow V_1 + V_2 = -V_{out}$$

# Voltage Follower

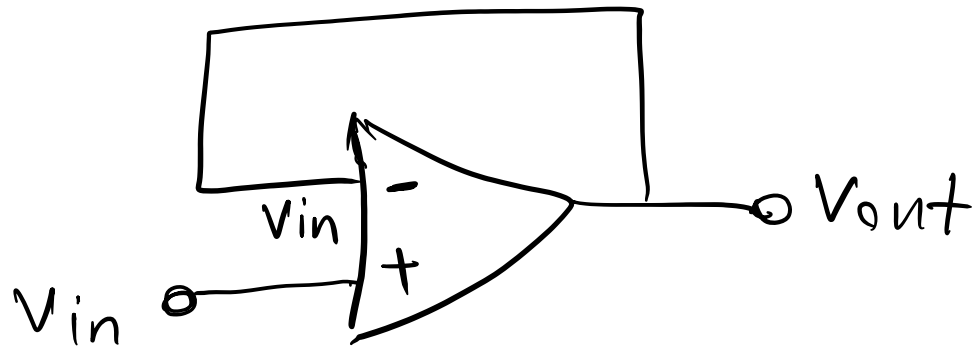


$$V_{out} = V_{in}$$

The voltage follower give effective isolation output from the input source to avoide overloading effect. (used in construction of buffers in logic circuits).

---


# Current to voltage Amplifier

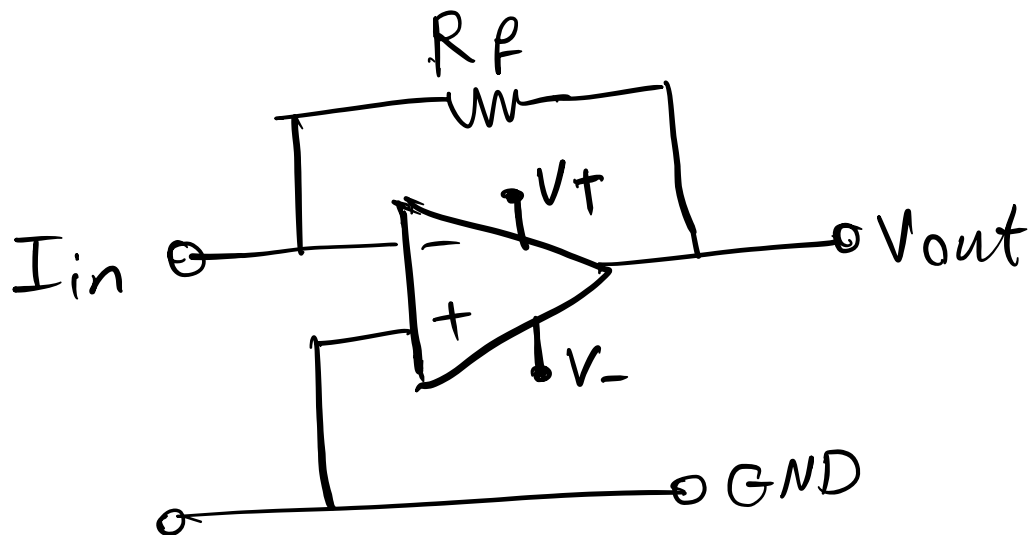

$$V_{out} = -I_{in} R_f$$

---

# Voltage to current amplifier

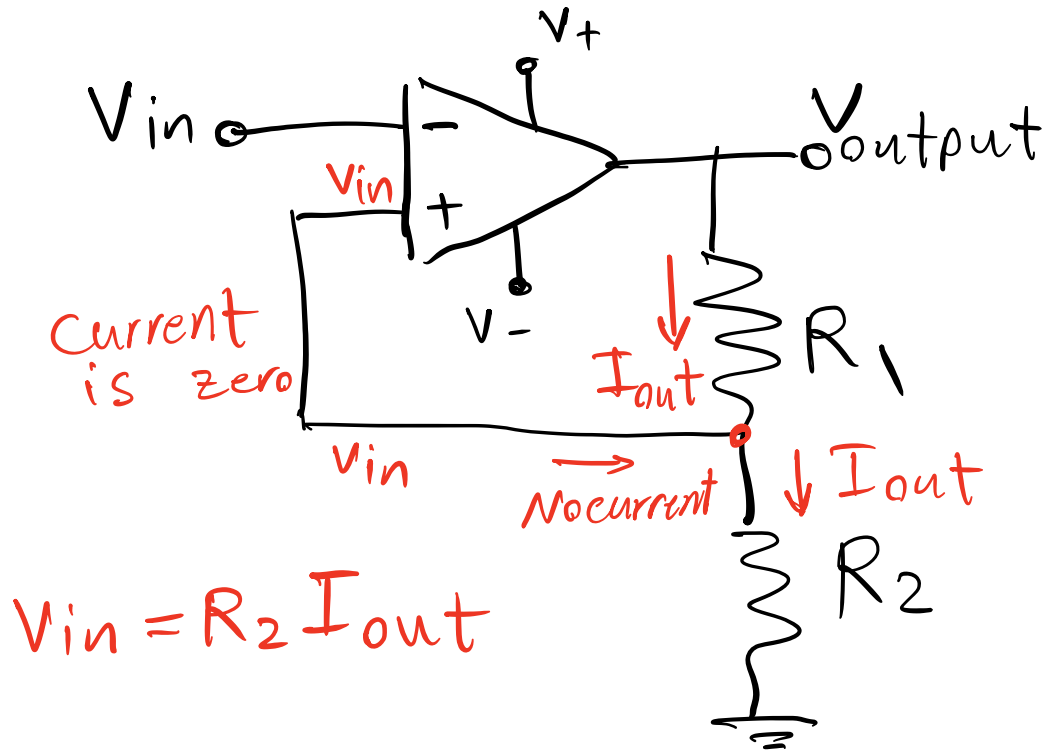


$$V_{in} = R_2 I_{out}$$

$$V_{out} - V_{in} = I_{out} (R_1)$$

$$V_{out} = I_{out} (R_1 + R_2)$$
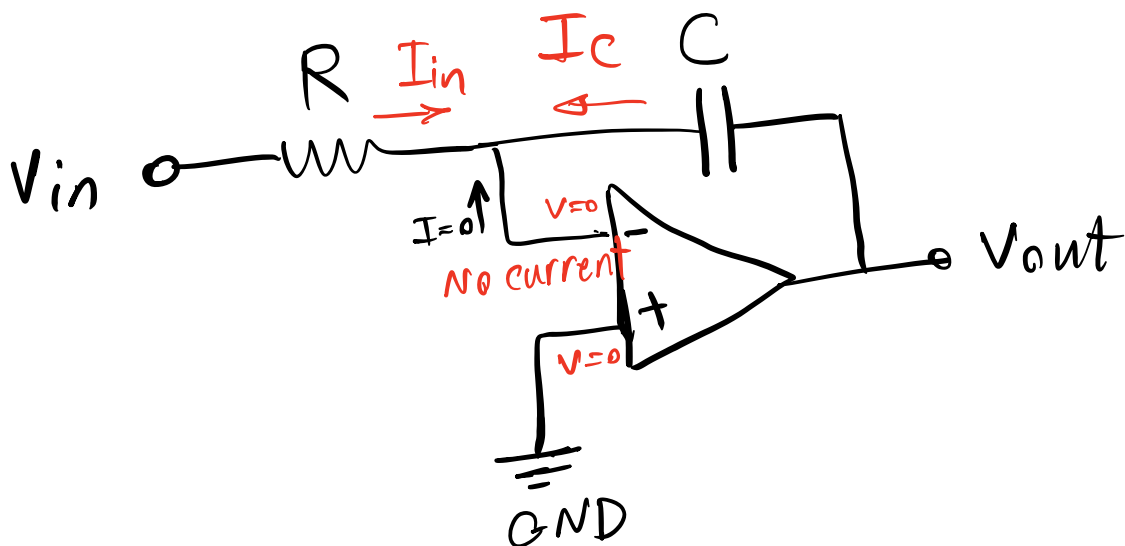
# Integrator circuits

For this circuit, all we have to do is to swap the capacitor and resistor in the previous circuit.



$$I_c + I_{in} = 0 \Rightarrow I_c = -I_{in}$$

$$I_c = C \frac{dV_{out}}{dt}$$

$$V_{in} = R I_{in}$$

$$I_{in} = \frac{V_{in}}{R}$$

$$C \frac{dV_{out}}{dt} = - \frac{V_{in}}{R}$$

$$\frac{dV_{out}}{dt} = - \frac{V_{in}}{RC}$$


$$dV_{out} = - \frac{V_{in}}{RC} dt$$

$$\int dV_{out} = - \int \frac{V_{in}}{RC} dt + \text{constant}$$

$$V_{out} = \int - \frac{V_{in}}{RC} dt + \text{constant}$$

---

## Differentiator circuit:

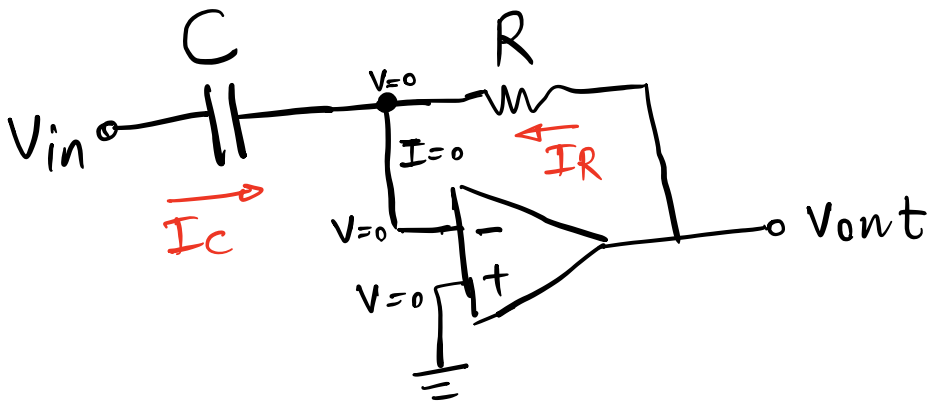

$$I_C = C \frac{dV_{in}}{dt}$$

$$I_R = \frac{V_{out}}{R}$$


$$I_R + I_C = 0$$

$$I_R = -I_C$$

$$\frac{V_{out}}{R} = -C \frac{dV_{in}}{dt} \Rightarrow V_{out} = -RC \frac{dV_{in}}{dt}$$



# Differential Amplifier

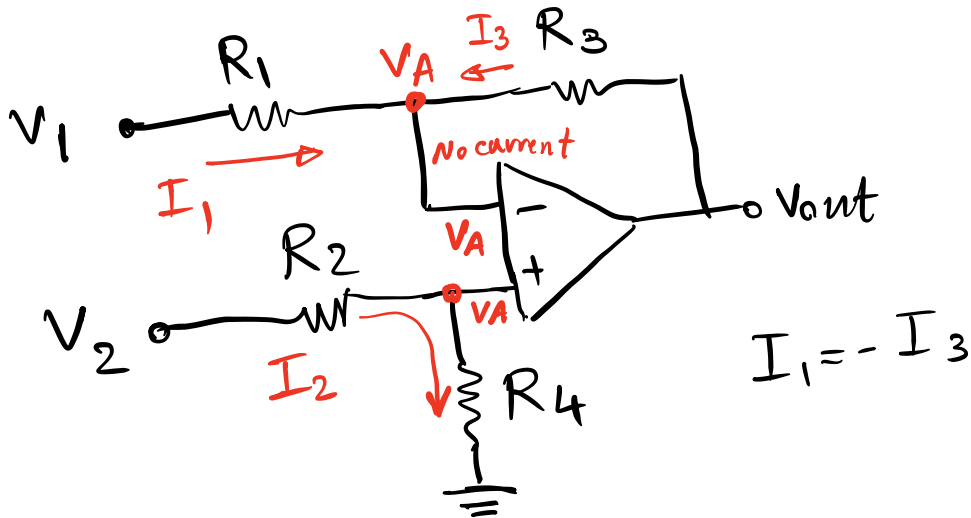

$$I_1 = \frac{V_A - V_1}{R_1}$$

$$I_3 = \frac{V_A - V_{out}}{R_3}$$

$$I_2 = \frac{V_2 - V_A}{R_2}$$

$$I_2 = \frac{V_A}{R_4}$$

$$\left\{ \begin{array}{l} \frac{V_A - V_1}{R_1} = - \frac{V_A - V_{out}}{R_3} \\ \frac{V_2 - V_A}{R_2} = \frac{V_A}{R_4} \Rightarrow \frac{V_2}{R_2} - \frac{V_A}{R_2} = \frac{V_A}{R_4} \end{array} \right.$$

$$\frac{V_2}{R_2} = V_A \left( \frac{1}{R_2} + \frac{1}{R_4} \right) \Rightarrow \frac{V_2}{R_2} = V_A \frac{R_2 + R_4}{R_2 R_4}$$

$$V_A = \frac{V_2}{R_2} \left( \frac{R_2 R_4}{R_2 + R_4} \right)$$

$$\frac{V_A - V_1}{R_1} = - \frac{V_A - V_{out}}{R_3}$$

$$\frac{V_A}{R_1} + \frac{V_A}{R_3} = \frac{V_1}{R_1} + \frac{V_{out}}{R_3}$$

$$V_A \left( \frac{R_1 + R_3}{R_1 R_3} \right) = \frac{V_1}{R_1} + \frac{V_{out}}{R_3}$$

$$V_A = \frac{V_2}{R_2} \left( \frac{R_2 R_4}{R_2 + R_4} \right)$$

$$\frac{V_2}{R_2} \left( \frac{R_2 R_4}{R_2 + R_4} \right) \left( \frac{R_1 + R_3}{R_1 R_3} \right) = \frac{V_1}{R_1} + \frac{V_{out}}{R_3}$$

$$V_{out} = V_2 \frac{(R_3 + R_1) R_4}{(R_4 + R_2) R_1} - V_1 \frac{R_3}{R_1}$$

Differential amplifier

Example:  $R_1 = R_2 = R_3 = R_4$

$$V_{out} = V_2 - V_1$$

Difference  
between input  
voltages  $V_1$   
and  $V_2$