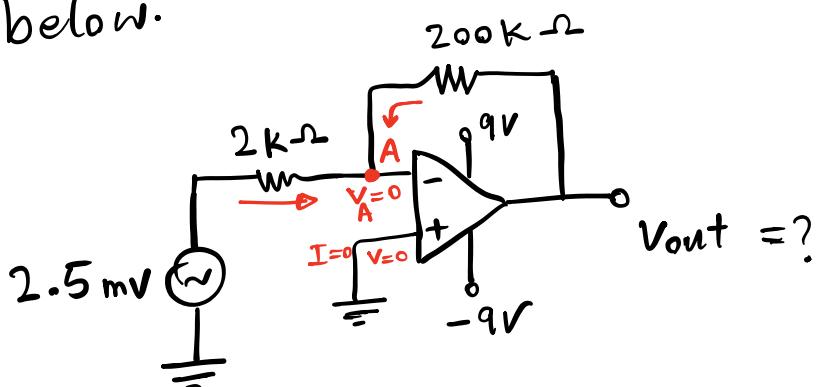


OP-Amp Examples


1- Find V_{out} in the OPAMP circuit below.



$$\frac{V_{out}}{200 \text{ k}\Omega} = -\frac{2.5 \text{ mV}}{2 \text{ k}\Omega}$$

$$V_{out} = -\frac{200 \text{ k}\Omega}{2 \text{ k}\Omega} 2.5 \text{ mV} = -250 \text{ mV}$$

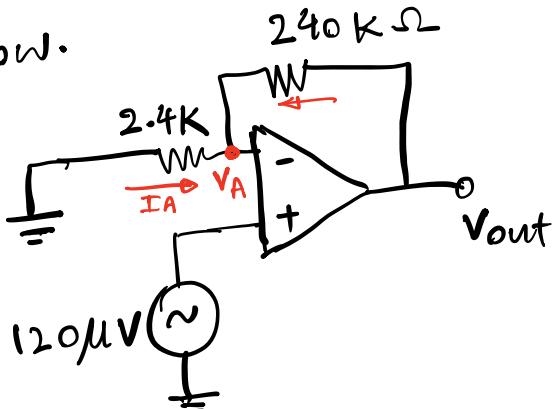2- Find V_{out} in the OP-Amp circuit below.




$$1 + \frac{240K^2}{2.4K^2} = 1 + 100 = 101$$

$$V_{out} = (101)(120 \mu V) = \frac{101 \times 120}{1000} mV$$

$$V_{out} = 12.12 mV$$

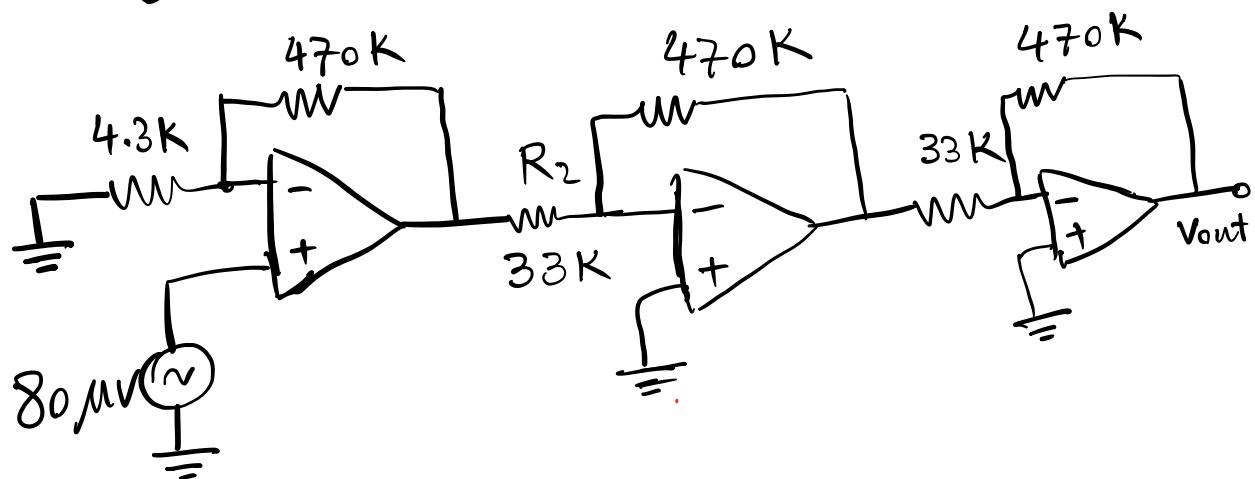3- Find V_{out} in the Op-Amp circuit below.




$$V_{out} = \left(1 + \frac{470}{4.3}\right) \left(-\frac{470}{33}\right) \left(-\frac{470}{33}\right) 80 \mu V$$

$$V_{out} = (110)(-14.2)(-14.2) 80 \mu V$$

$$V_{out} = 22.2 \times 10^3 \times 80 \mu V = 1.78 V$$

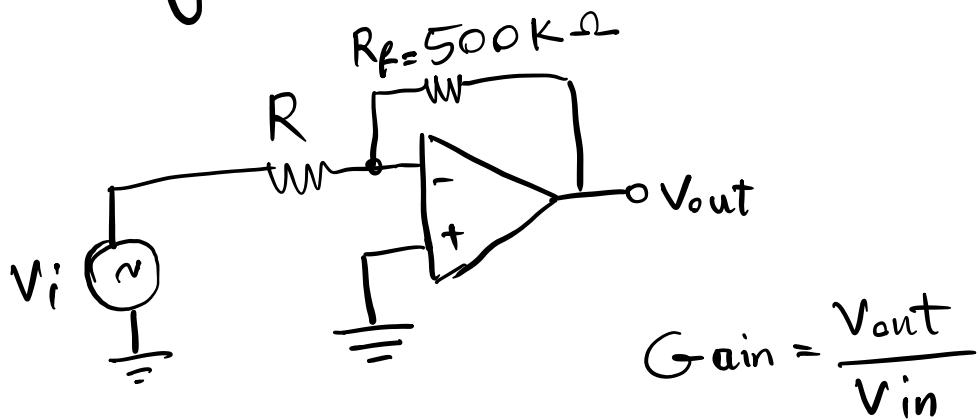4- Find the resistor value R for a gain of -10, -20, and -50.




$$\frac{V_{out}}{R_f} = -\frac{V_i}{R} \Rightarrow \text{Gain} = -\frac{R_f}{R}$$

$$-10 = -\frac{500}{R} \Rightarrow R = 50 K\Omega$$

$$-20 = -\frac{500}{R} \Rightarrow R = 25 K\Omega$$

$$-50 = -\frac{500}{R} \Rightarrow R = 10 \text{ k}\Omega$$

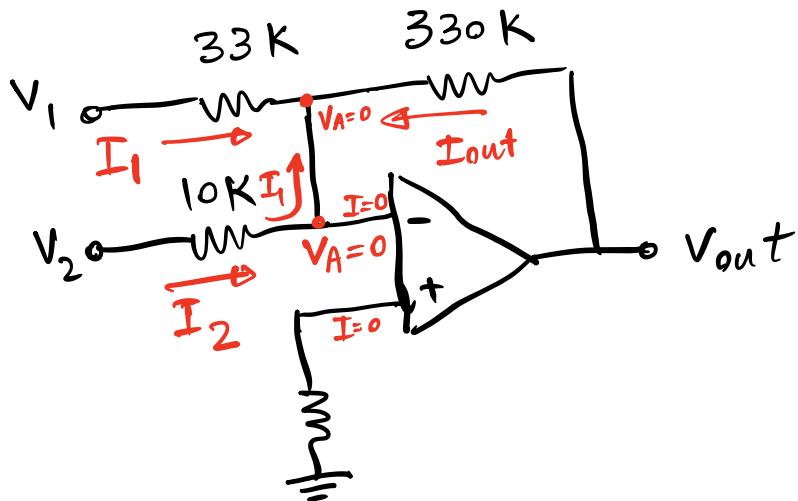5- Find V_{out} in the summing op-Amp
in the circuit below.




$$I_1 + I_2 = -I_{out}$$

$$\frac{V_1}{33K} + \frac{V_2}{10K} = -\frac{V_{out}}{330K}$$

$$V_{out} = -330 \left(\frac{V_1}{33} + \frac{V_2}{10} \right)$$

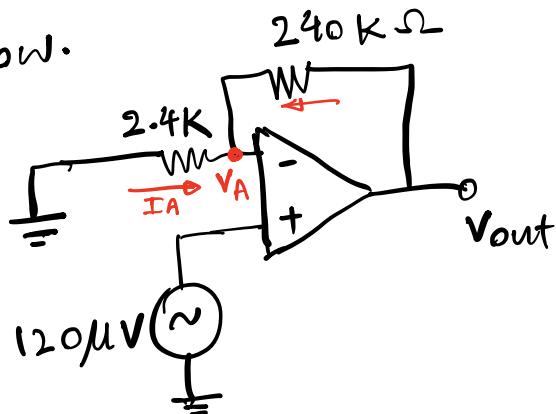- Find V_{out} in the op-Amp circuit below.



$$V_A = 120 \text{ mV}$$

$$\frac{120 \text{ mV}}{2.4 \text{ K}\Omega} = - \frac{120 \text{ mV} - V_{out}}{240 \text{ K}\Omega}$$


$$V_{out} = 240 \text{ K} \left(\frac{120 \text{ mV}}{2.4 \text{ K}} + \frac{120 \text{ mV}}{240 \text{ K}\Omega} \right)$$

$$V_{out} = 240 \text{ K} \left(\frac{100}{2 \text{ K}} \text{ mV} + \frac{1}{2 \text{ K}} \text{ mV} \right)$$

$$V_{out} = 120 (100 + 1) \text{ mV} = 120 (101) \text{ mV}$$


$$= 12.12 \text{ mV}$$

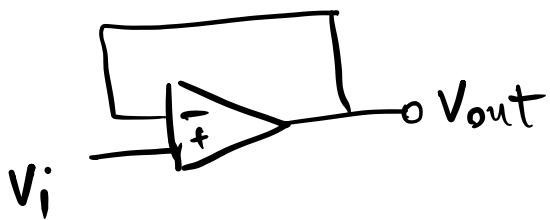6 - Find V_{out} in the voltage follower below.



$$V_{out} = V_i$$

7- Find I and V_{out} .

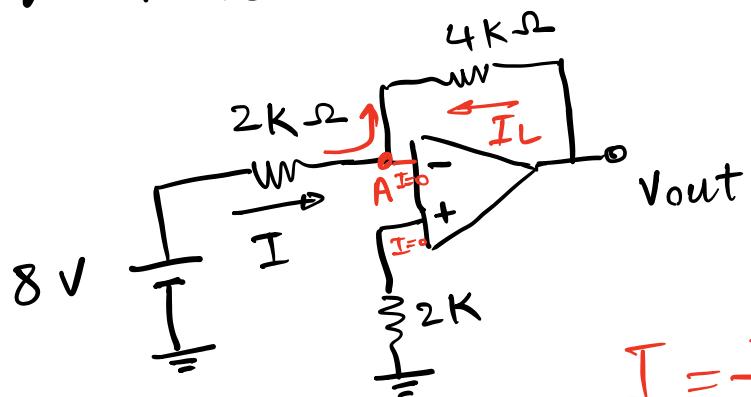


$$I = -I_L$$

$$V_A = 0$$

$$\frac{8V}{2k\Omega} = -\frac{V_{out}}{4k\Omega} \Rightarrow V_{out} = -16V$$


8 - Find V_{out} .

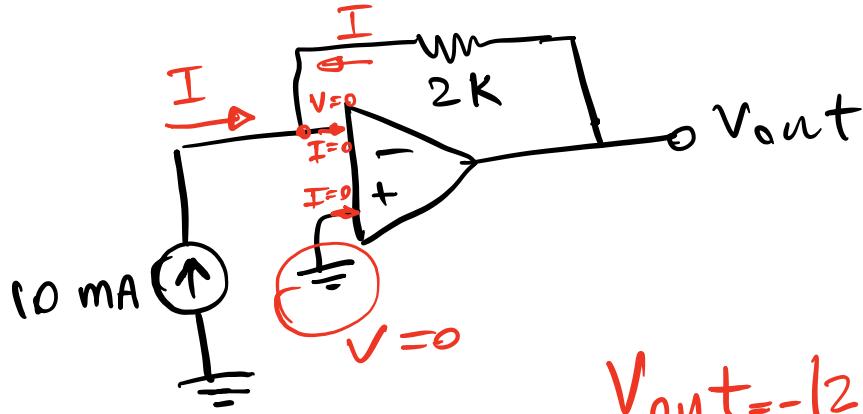

$$V_{out} = -(2 \text{ k})(10 \text{ mA})$$

$$V_{out} = -20 \text{ V}$$

9 - Find V_{out} .

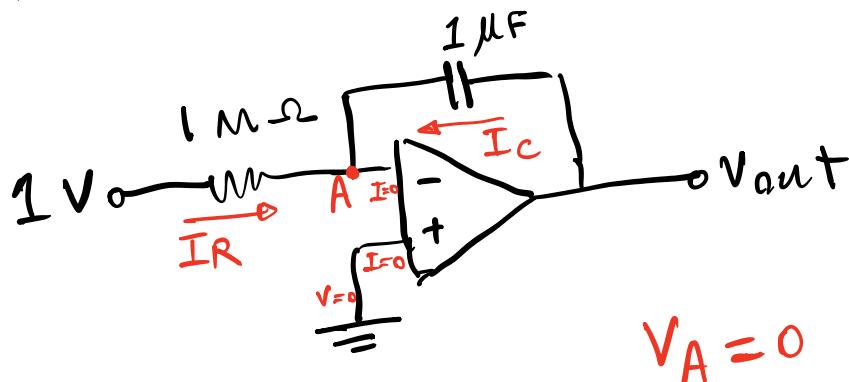

$$V_A = 0$$

$$I_C = -I_R$$

$$I_C = C \frac{dV_{out}}{dt}$$

$$I_R = \frac{V_{in}}{R} = \frac{1 \text{ V}}{1 \text{ M}\Omega}$$

$$C \frac{dV_{out}}{dt} = - \frac{V_{in}}{R}$$

$$V_{out} = - \frac{1}{RC} \int V_{in} dt$$

$$V_{out} = \frac{-1}{(1 \text{ m}\Omega)(1 \mu\text{F})} \int I dt$$

$$V_{out} = -1 (10^{-6})(10^6) \int dt$$

$$V_{out} = -t$$

