

**Cal Poly Pomona
ECE Dept.**

ECE 2300L

Lab # 8

Dr. Rafi

Prelab

Design a 2732-based EPROM system to display square of a BCD digit on seven segment displays. Use a minimum number of 74LS47 BCD to seven segment converters. Each BCD digit will be input to the EPROM via DIP switches.

LAB

Parts List: Determine the required parts.

Implement the above circuit , and demonstrate its operation.

Postlab

1. What is the basic differences between :

- (a) Volatile and nonvolatile memories.**
- (b) EPROM and EEPROM.**
- (c) SRAM and DRAM.**
- (d) PLD and ROM.**
- (e) CPLD and FPGA.**

2. Draw block diagrams showing enamel, address, and data lines for each of the following: 2732, 2764, 27128, and 27256.

3. Draw a schematic for a 6k X 8-bit memory array using a minimum number of 2732's. What are the highest and the lowest memory addresses (in hex) in the array?